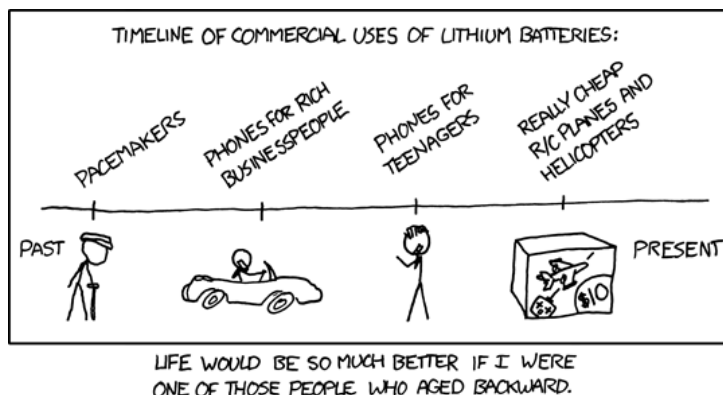


Circuit Lab C - Regionals



Directions

- Each team will be given **50 minutes** to complete the test.
- There are four sections: **History, Multiple Choice, Short Answer, Free-Response.**
- Do not worry about significant figures. Just make sure to **use 3 or more in your answers** *unless otherwise specified*.
- Also, it is not necessary to show work to receive full credit. However, partial credit may be given if the final answer is incorrect, but sufficient work is shown.
- Tiebreakers, in order: Free-Response Section Score, Multiple Choice Section Score, Short Answer Section Score, FRQ6, FRQ5 ... FRQ1.
- Best of luck! And may the odds be ever in your favor.
- Per Texas Science Olympiad rules, you must have printed notes for this event. If you are communicating with your partner through a voice or video call, please start it before you begin the test itself.

Significant time spent outside of the browser window is grounds for a penalty or disqualification per TSO policies.

1. (0.01 pts)

By selecting True for this question, we confirm that for the duration of this exam, we will abide by all Science Olympiad rules, will not communicate with any person except our partner and the event supervisors, will not access the internet or use any resources not explicitly permitted by the official 2021 Science Olympiad rules manual for this event.

We understand that if we violate any of the above, we will likely be disqualified for this event, and will incur adverse effects on both ourselves and our team. Furthermore, we would be violating the spirit of Science Olympiad.

Please do not submit without answering this question.

☒ True ☐ False

History

All questions in this section are worth 1 point each, with the exceptions of 9 and 13, which are worth 2 points each.

Please follow the instructions for the Fill-In-The-Blank questions carefully.

For the next six questions, answer with one of the following: Ampere, Coulomb, Kirchhoff, Volta, Ohm, Tesla, or Faraday, spelled and capitalized exactly as written here

Names may or may not be repeated.

2. (1.00 pts) The unit of charge bears my name.

Coulomb

3. (1.00 pts) I discovered induced current.

Faraday

4. (1.00 pts) The law relating V, I, and R bears my name.

Ohm

5. (1.00 pts) I found that "The algebraic sum of currents in a network of conductors meeting at a point is zero."

Kirchhoff

6. (1.00 pts) I created the first induction motor.

Tesla

7. (1.00 pts) I discovered that a wire with flowing current attracts other nearby wires. I also made a law that described this phenomenon quantitatively.

Ampere

This set of questions deals with a scientist, and his setup using a torsion balance to quantitatively measure electrical charges.
(This setup involves a bar suspended on a tension fibre with a charge on either end, as well as another charge fixed in place)

8. (1.00 pts) What is the name of this scientist (use the Name bank from the first six questions)

Coulomb


9. (2.00 pts) Explain how a torsion balance is used to make measurements?

Expected Answer: The force on the torsion balance causes it to twist, and oscillate. This oscillation can be measured, and the force can be calculated. (half points if no mention of oscillation).

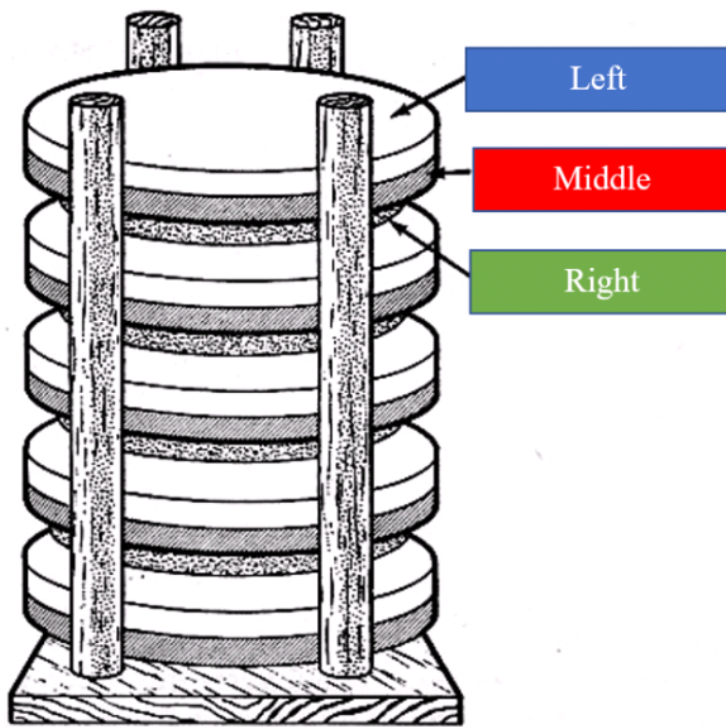10. (1.00 pts) Write down the equation for the law that was found using this experiment.

Expected Answer: $F = kQq/r^2$

This set of questions deals with the scientist who created this contraption:



11. (1.00 pts) What is this?

Expected Answer: Voltaic Pile/First Battery

12. (1.00 pts) Which scientist first made this? (use the Name bank from the first six questions)

Volta

13. (2.00 pts) What are the Blue, Red, and Green labels referring to?

Zinc

Copper

Cardboard soaked in weak


Multiple Choice

14. (2.00 pts) A 100 volt battery is in series with a 25 ohm resistor. What is the current going through the resistor?

- ☐ A) 2500 A
- ☐ B) 125 A
- ☐ C) 100 A
- ☐ D) 25 A
- ☒ E) 4 A

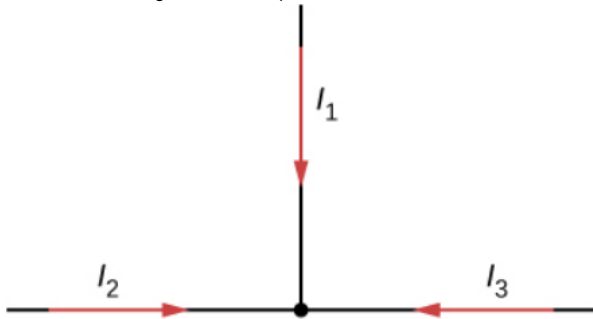
15. (2.00 pts)

Which of the following conditions is possible?



- ☐ A) All three currents are positive
- ☒ B) All three current are zero
- ☐ C) One current is zero, the other two are negative.
- ☐ D) The bottom two currents are equivalent. The vertical current is zero.
- ☐ E) None of the above are possible.

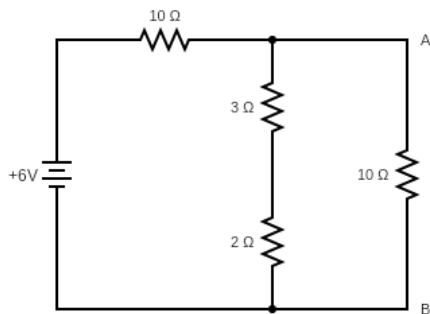Use the following circuit diagram for the next three questions



16. (2.00 pts) What is the total equivalent resistance of the above circuit?

- ☒ A) 13.3 Ω
- ☐ B) 4.5 Ω
- ☐ C) 3.3 Ω
- ☐ D) 5.3 Ω
- ☐ E) 25 Ω

17. (2.00 pts) What is the voltage at point A?

- ☐ A) 4.5 V
- ☐ B) .9 V
- ☐ C) 6 V
- ☐ D) 0 V
- ☒ E) 1.5 V

18. (2.00 pts) As viewed from nodes A and B, what is the Norton equivalent current of this circuit?

- ☐ A) 0.45 A
- ☒ B) 0.6 A
- ☐ C) 1.5 A

- ☐ D) 1.8 A
- ☐ E) 2.4 A

19. (2.00 pts)


A and B are the inputs to a logic gate, whose truth table is given below. What type of logic gate is this?

A	B	Output
T	T	F
T	F	T
F	T	T
F	F	F


- ☐ A) AND
- ☐ B) OR
- ☐ C) NAND
- ☐ D) NOT
- ☒ E) XOR

20. (2.00 pts) Which of the following is NOT a low-pass filter

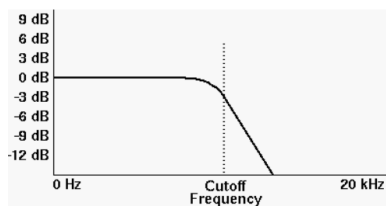A) A circuit with the following frequency-response graph below.




B)

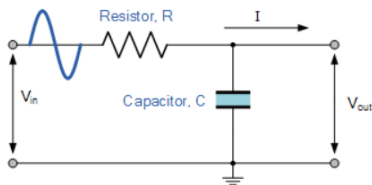


C) A circuit that allows DC current to pass unimpeded, but not high frequency AC current.

D)

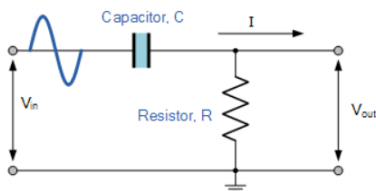

E)

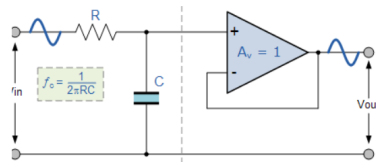

- ☐ A) A
- ☐ B) B
- ☐ C) C
- ☒ D) D
- ☐ E) E

21. (2.00 pts)

A wire is formed into a coil of length 2 cm, with 100 turns. A current of 2.5 A is run through it. What is the magnetic field in the center of the coil? Assume a total vacuum.

- ☐ A) 5 T
- ☐ B) .0016 T
- ☐ C) .31 T
- ☒ D) .16 T
- ☐ E) .0031 T

22. (2.00 pts) Which of the following elements would be present on the n side of a p-n junction?

- ☐ A) Nitrogen
- ☒ B) Antimony
- ☐ C) Aluminum
- ☐ D) Boron
- ☐ E) Sodium

23. (2.00 pts) What are the specifications of current supplied from American sockets?

- ☐ A) 110 V, 50 Hz
- ☒ B) 110 V, 60 Hz
- ☐ C) 220 V, 50 Hz
- ☐ D) 220 V, 60 Hz
- ☐ E) 230 V, 60 Hz

24. (2.00 pts) Which of the following boolean algebra expressions yield this truth table?


P	Q	R	A
T	T	T	F
T	T	F	F
T	F	T	T
T	F	F	F
F	T	T	T
F	T	F	F
F	F	T	T
F	F	F	F

I. $(\overline{PQ} + P\overline{Q})(R + PQ)$

II. $(\overline{PQ} + P\overline{Q})(R + PQ)$

III. $R(\overline{PQ})$

- ☐ A) I only
- ☐ B) III only
- ☐ C) I and II only
- ☒ D) I and III only
- ☐ E) I, II, and III

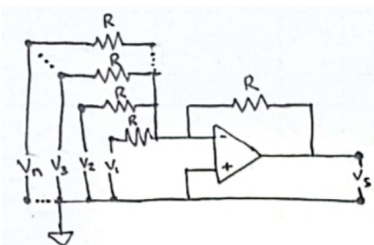25. (2.00 pts) V_s is given by which of the following expressions

- ☒ A) $V1 + V2 + V3 + \dots + Vn$
- ☐ B) $\frac{1}{\frac{1}{V1} + \frac{1}{V2} + \frac{1}{V3} + \dots + \frac{1}{Vn}}$
- ☐ C) $-(V1 + V2 + V3 + \dots + Vn)$
- ☐ D) $V1 * V2 * V3 * \dots * Vn$
- ☐ E) $\frac{-1}{\frac{1}{V1} + \frac{1}{V2} + \frac{1}{V3} + \dots + \frac{1}{Vn}}$

26. (2.00 pts) Which of these resistor arrangements would yield the lowest overall resistance?

- ☐ A) Large resistors in parallel
- ☐ B) Large resistors in series
- ☒ C) Small resistors in parallel
- ☐ D) Small resistors in series
- ☐ E) Large and small resistors in series

27. (2.00 pts) Gallium Phosphide is NOT used in LEDs of which color

- ☐ A) Red
- ☒ B) Blue
- ☐ C) Orange
- ☐ D) Green
- ☐ E) Yellow

28. (2.00 pts) Which is not a reason circuit diagrams do not accurately represent real phenomena?

- ☐ A) Resistance of a component changes as it heats up
- ☐ B) Energy is lost as heat
- ☐ C) Batteries do not have constant voltage
- ☐ D) Wires have resistance
- ☒ E) Circuit analysis laws are only theoretical; they do not apply to real circuits

29. (2.00 pts) A fully discharged 2.7 μ F capacitor is in series with a 9.6V battery and a 330 k Ω resistor circuit. The capacitor charges _____.

- ☐ A) Fully in 0.891 seconds
- ☒ B) ~63% in 0.891 seconds
- ☐ C) Fully in 0.944 seconds
- ☐ D) ~63% in 0.944 seconds
- ☐ E) None of the above

30. (2.00 pts) Which is an advantage AC has over DC?

- ☐ A) It's safer
- ☒ B) It's transmitted easily over long distances
- ☐ C) It's easily stored
- ☐ D) It requires fewer transmission lines
- ☐ E) None

31. (2.00 pts) If a positively charged particle is traveling east, what direction is the magnetic force on it? Assume the Earth's magnetic field is oriented with geographic north.


- ☐ A) South
- ☐ B) North
- ☐ C) West
- ☐ D) Down
- ☒ E) Up

Use the diagram below to answer the next two questions:



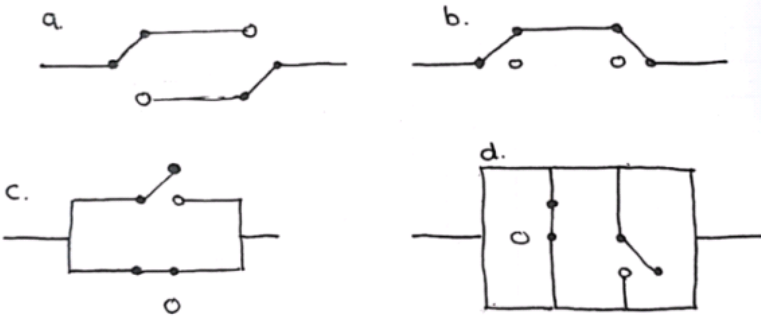32. (2.00 pts)


For this question, assume that terminals **A** and **B** are connected with a bulb. Which of the following configurations would be necessary, between **1** and **2** to be able to toggle the bulb using either switch, from any configuration?



- ☒ A) A
- ☐ B) B
- ☐ C) C
- ☐ D) D
- ☐ E) None of the options

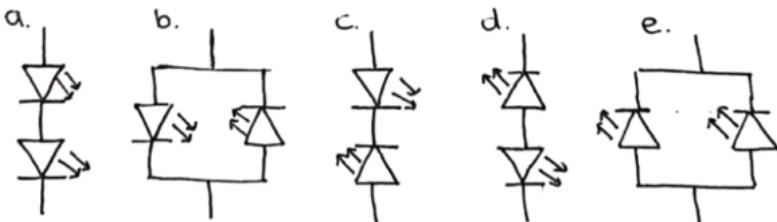33. (2.00 pts)

For this question, assume that terminals **1** and **2** are shorted. Which of the following LED configurations, between terminals **A** and **B** would guarantee that at least one LED would shine, even if the polarity of the battery was flipped?



- ☐ A) A
- ☒ B) B
- ☐ C) C
- ☐ D) D
- ☐ E) E

Short Answer

34. (2.00 pts)

If you wish to connect capacitors to maximize their overall capacitance, how would you connect them? What if you wanted to connect resistors to maximize their effective resistance?

Expected Answer: Parallel; Series (one point for each)

35. (3.00 pts)

I want to decrease the resistance of a copper bar.

Should I increase, decrease, or ignore (ignore if it has no effect) each of the following?

Left: Temperature

Middle: Length

Right: Area

(Your choices are: Increase, Decrease, Ignore exactly as spelled and capitalized here)

Decrease

Decrease

Increase

36. (2.00 pts)

Explain the role of a commutator in a DC motor


Expected Answer: It acts to rectify the current direction flowing through the motor. It transfers current from the brushes to the windings

37. (2.00 pts)

At what AC current threshold does one experience paralysis?

Expected Answer: 10-16 mA

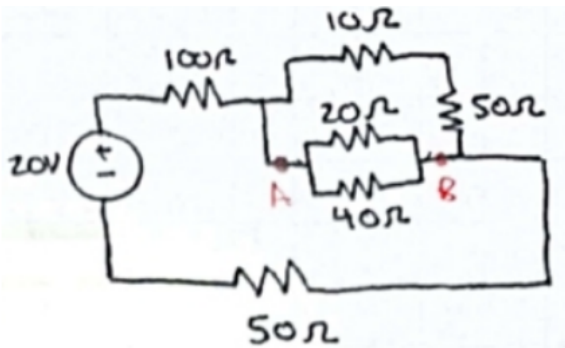Consider the following circuit diagram for the next 3 questions



38. (2.00 pts)

What is the current going through the 100 ohm resistor, in mA? (round to the nearest 10 mA, do not write the unit)


120

39. (2.00 pts)

What is the voltage drop across the 50 ohm resistor on the bottom of the circuit, in V (round to the nearest .1 V, do not write the unit)

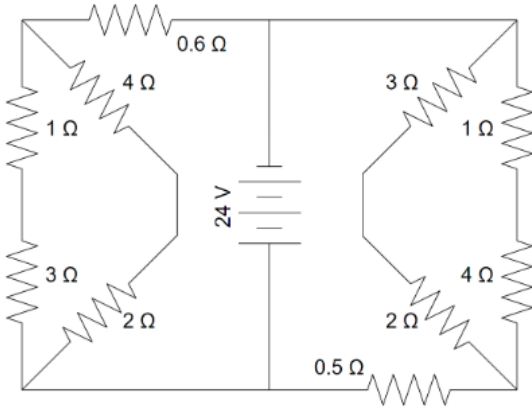40. (2.00 pts) What is the power dissipated between nodes A and B, in mW (round to the nearest 10 mW, do not write the unit)?

Use the following circuit diagram for the next 3 questions (round to two decimal places or add trailing zeroes to two decimals, no unit)



41. (2.00 pts) Compute the total equivalent resistance of the above diagram, in Ohms (Hint: redraw it!)

42. (2.00 pts) Determine the current running through the .6 Ohm resistor

43. (2.00 pts) What is the power consumed by the entire circuit, in W?

Free-Response


Point-values vary throughout this section.

Please show as much work as you can (We know its hard online). We want to give you as much credit as we can, and showing us your work makes it easier for us to do that.

FRQ1


1. Find the equivalent capacitance of the infinite ladder of capacitors below, if $C = 1 \text{ F}$.

Hint: Observe the circuit made by taking all capacitors to the right of nodes D and E. Compare this to your original circuit.

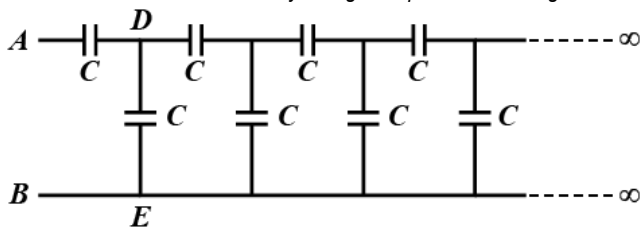

FRQ2

Consider the following circuit diagram.

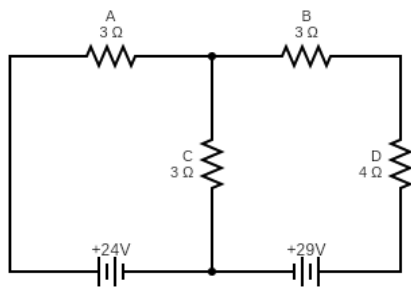

44. (3.00 pts) What is the current running through resistor C?

Expected Answer: 5 A

45. (3.00 pts) What is the voltage drop across resistor A?


Expected Answer: 9 V

46. (1.00 pts) What current law helps us understand this circuit?

Expected Answer: Kirchhoff Loop Rule Kirchhoff Voltage Law (KVL) Kirchhoff Second Law

FRQ 3

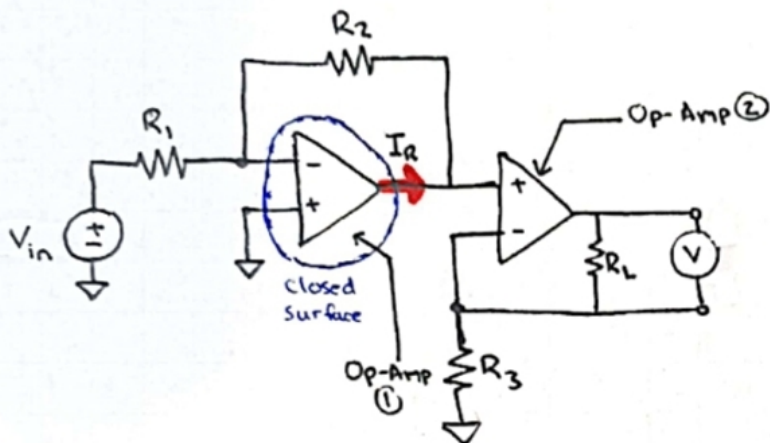Here, we will analyze the following Op-Amp circuit. $R_1 = 100$ ohms, $R_2 = 300$ ohms, $R_3 = 50$ ohms, $R_L = 1000$ ohms, and $V_{in} = 10$ V. (assume ideal op-amps)



47. (1.00 pts) What approximations can you make about the voltages of the input terminals for ideal op-amps, as well as the current flowing into these terminals?

Expected Answer: The voltages at the two input terminals are the same. There is negligible current flowing into the input terminals

48. (2.00 pts) What is the current represented by the red arrow (I_R) in milliamps?

Expected Answer: 100 mA

49. (3.00 pts)

KCL would suggest that there should be no current flowing into or out of the closed surface given by the blue circle and that since no current flows into the input terminals of Op-Amp ①, the current in the red arrow (I_R) should be 0. What is wrong with this argument?

Expected Answer: The op-amp symbol is simplified. There are actually more terminals that connect to the op-amp, which actually deliver the power. Once these are included, Kirchhoff's laws are not actually violated.

50. (3.00 pts) What is the voltage at the negative terminal of Op-Amp ② (remember your answer to 47)?

Expected Answer: -30 V

51. (3.00 pts) What does the voltmeter read?

Expected Answer: - 600 V


52. (4.00 pts)

What is the power gain of this circuit (that is, how many times more power is dissipated in R_L than is given by the voltage source V_{in} ? Don't worry about conservation of energy; your answer to 49 should have addressed this!)

Expected Answer: 360

FRQ 4

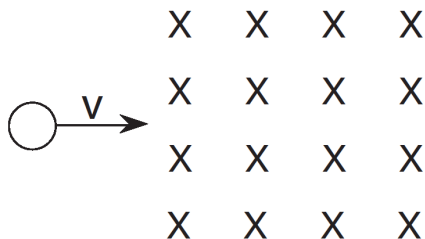Consider the motion of the electron as shown below. The uniform magnetic field is of strength .4 T and the particle moves at 200 m/s. The charge of an electron is -1.602×10^{-19} coulombs



53. (3.00 pts) Calculate the magnitude of the force exerted on the particle, in N.

Expected Answer: 1.28×10^{-17} N

54. (3.00 pts) At the first instance the particle enters the field, what direction is the applied force? Explain.

Expected Answer: Down. Using the left-hand rule (or opposite of right-hand rule), we can see the force is downwards

55. (3.00 pts) If the particle is observed over a length of time, describe the path the particle takes.


Expected Answer: The particle forms a semicircle/circle in the field.

56. (3.00 pts) Scientists can make use of this kind of particle motion. Name the apparatus that utilizes the phenomenon seen in this question, and explain what data it can provide.

Expected Answer: Mass spectrometer. Provides mass/charge ratios, used to identify molecular weights or quantify unknown compounds.

FRQ 5

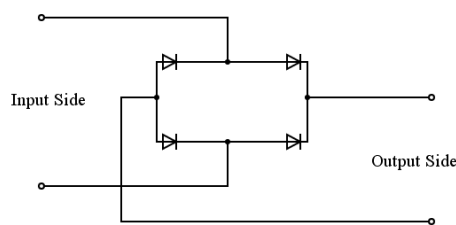Use the following diagram for this question



57. (2.00 pts) What is the above circuit used for?

Expected Answer: This circuit is used to rectify AC current into DC current.

58. (3.00 pts) In practical use, the setup shown above is inefficient. Explain the inefficiency.

Expected Answer: The voltage is not maintained; it drops to 0 when the AC current reaches 0 V.

59. (3.00 pts) What is the simplest and most common modification that can improve it? Explain what is changed, and where.


Expected Answer: Addition of a capacitor across the output side.

FRQ 6

In this problem, we assume a standard x-y grid. At some distance $+D$ and $-D$ along the x-axis, there are two fixed particles A and B, each with charge $+Q$. Now, there is another particle C with charge $-q$, constrained to move along the y-axis.

We will show in this problem that for some conditions, particle Z approximates a simple harmonic oscillator (like a pendulum moving at small angles, or a mass-spring system).

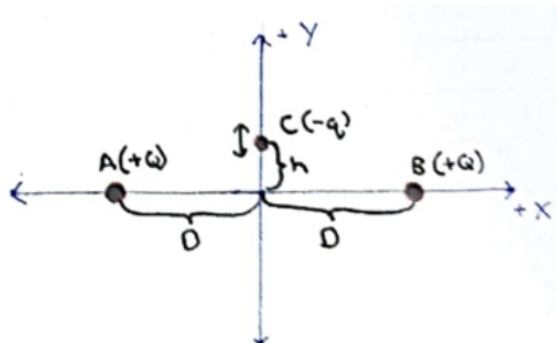Hint: The defining feature of SHM (simple harmonic motion) is that the restoring force $F = -Kr$, where r is the distance from equilibrium, and k is a constant of proportionality (not to be confused with Coulomb's constant, k).



This is a fairly difficult, but satisfying problem. Unless you've seen this before, I would recommend solving other problems before attempting this one.

60. (2.00 pts) Qualitatively or quantitatively argue that when C is at the origin, the system is in equilibrium.

Expected Answer: Symmetry, or just using Coulombs to show that overall force felt by C is 0, if at origin

61. (2.00 pts) What is the distance R between C and either A or B, in terms of h and D?

Expected Answer: $R = \sqrt{h^2 + D^2}$

62. (3.00 pts)

Find the force (negative if towards the origin, positive if away) felt by the particle C if it is at some non-zero displacement h from the origin, in terms of k\$, Q, q, h, and R?

Expected Answer: $F = -2kQqh/R^3$

63. (3.00 pts)

For small displacements h, make an approximation for the distance between the particle C and each of the positive charges (in other words, make an approximate relation between R and D, for small values of h).

Hint: think about what happens to the "h" term.

Expected Answer: $R \sim D$ (h vanishes)

64. (4.00 pts) Using your approximation, show that for small displacements, C approximately follows simple harmonic motion.

Expected Answer: Substituting the approximation, the force becomes $F = -2kQqh/d^3 = -(2kQq/d^3)h$, which is a (negative) constant times displacement

!!! Congratulations on finishing the test !!!

Written by:

Pranit Mohnot, pranit_mohnot@berkeley.edu

Kiran Thirukonda, k.thirukonda@utexas.edu

If you have any feedback about any of the exams at this tournament, please let us know through this form: <https://tinyurl.com/utreg21feedback> (<https://tinyurl.com/utreg21feedback>)

